Inputs: S, M1, D

Outputs: L, A

## Pre-Lab 2

S	M1	D	L	Α
0	0	0	0	0
0	0	1	0	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1_	1
1	1	1	1	0

